

DHT Pre-amplifiers

Alejandro Moglia


ETF.18 @Bellême, Nov 2018




An unorthodox approach...

Purpose of today

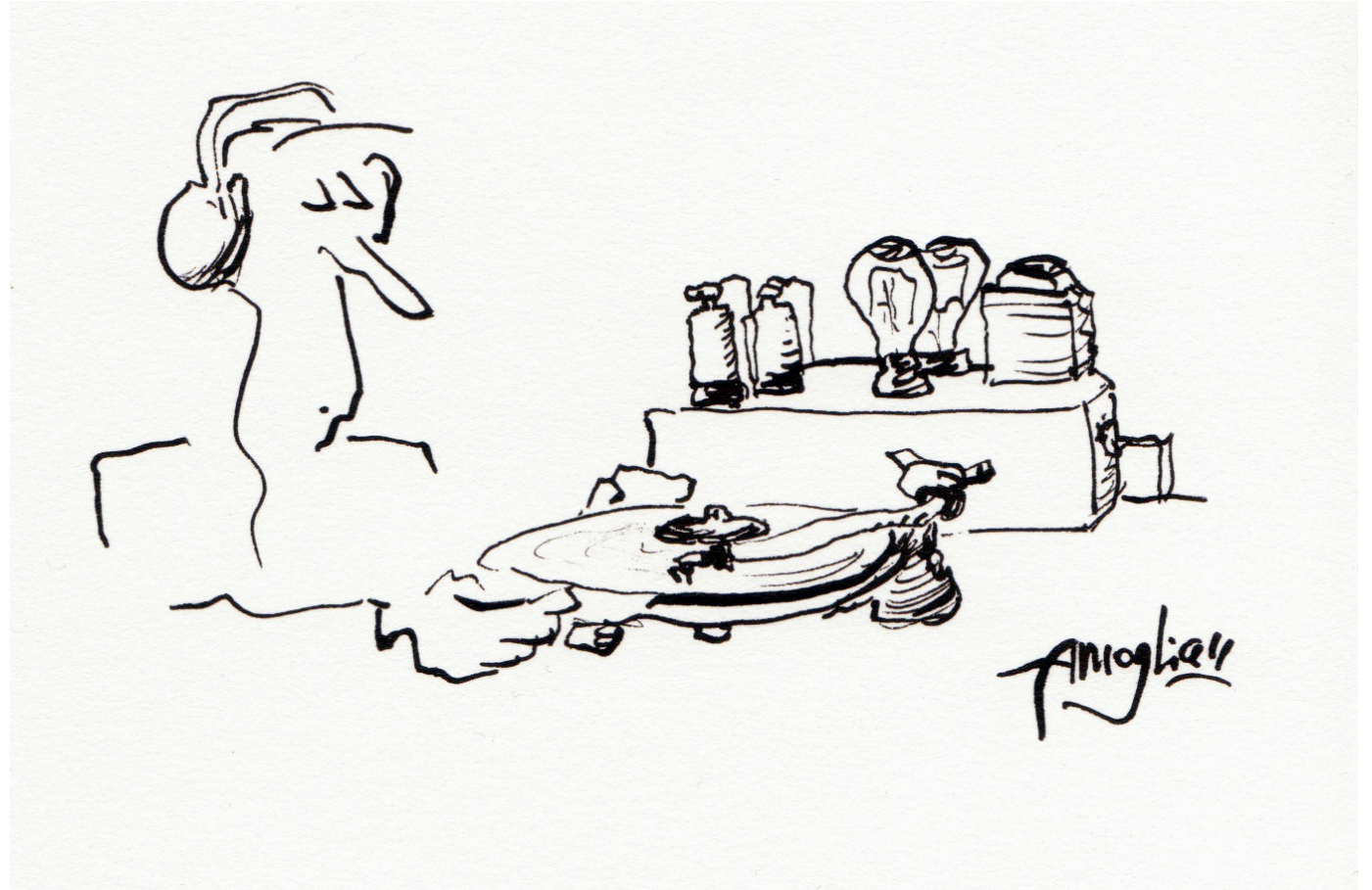Sharing my experience on DHT
preamps throughout my long
journey in combining quite a
lot of sand in hollow circuits



About Myself

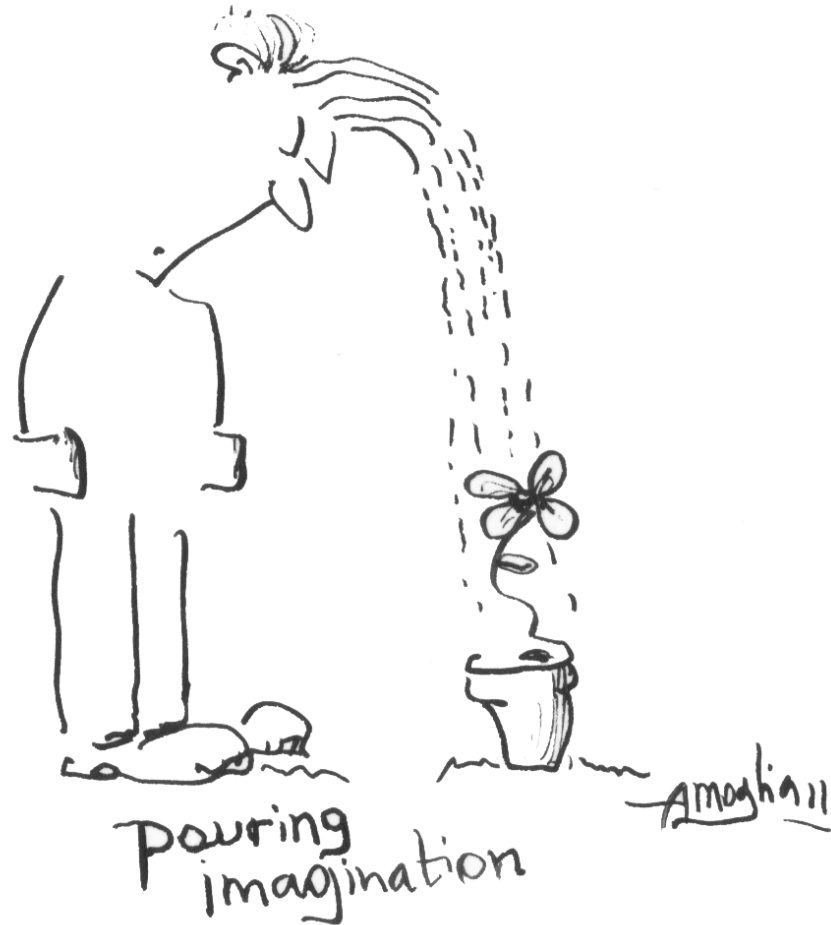

- Background
- Hobbies
- Audio


Why DHT in Pre-amps?

What we can hear

- Timbre
- Detail
- Distortion
- 3D image


What we can measure

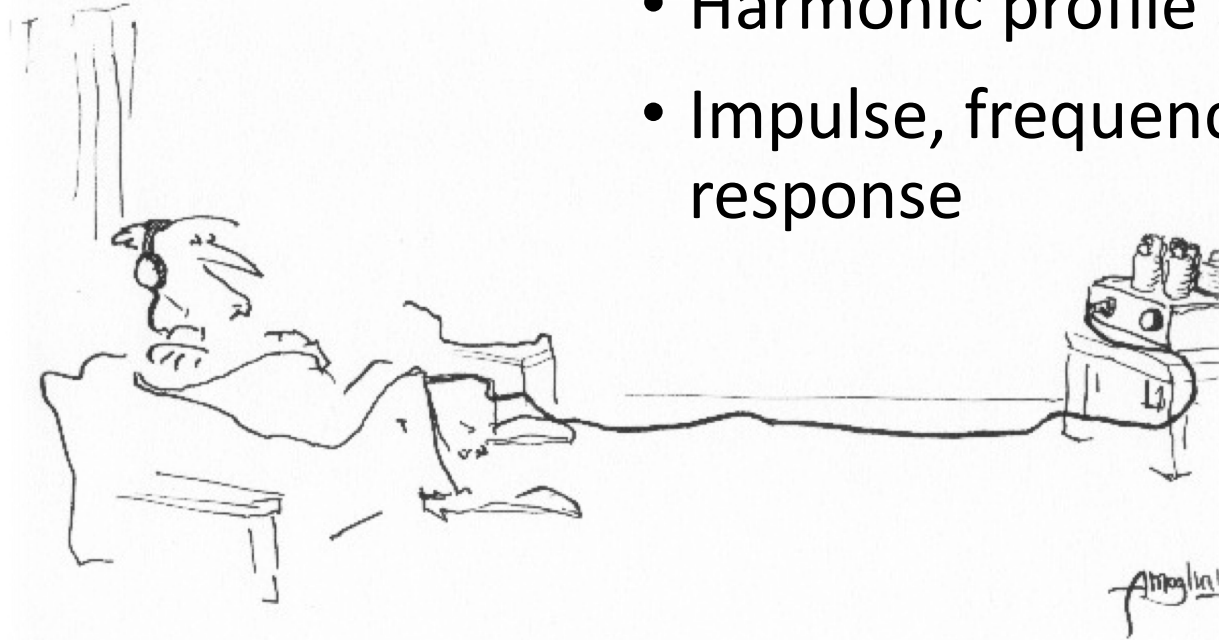- THD and IMD
- Harmonic profile
- Impulse, frequency & phase response



Closeness

The Traditional Approach

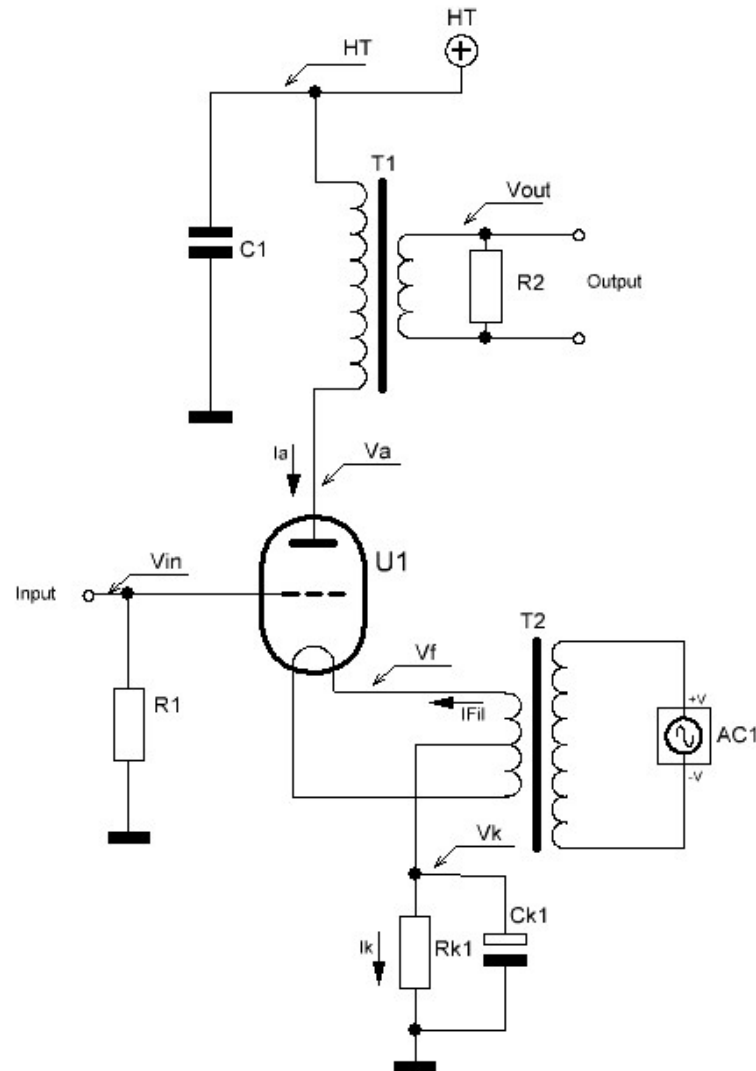

- Advantages
 - Lower gain and output impedance
 - Simplicity
 - Galvanic isolation
- Disadvantages
 - Quality of OPT
 - PS isolation
 - Heater IM distortion
 - Cathode cap

The DHT Pre-amp Challenges

- Microphonic noise
- Hum
- Power supply complexity
- Load demands
- Bias arrangement
- Weight, heat and space!
- Gain (too much or too little)
- The DHT itself – cost, age, etc.




What I've Learnt Over The Years


- What goes in the cathode is as important (or more than) as the anode load
 - Filament bias
 - SiC Diodes
- Filament supply
 - DC regulators
 - Choke input raw PSU
 - Filament starvation
- Keeping the noise down
 - Ground scheme and layout
 - Multi-chassis
 - Microphonic noise
- My preferred topologies and anode loads
 - Hybrid μ -follower (aka Gyrator)
 - Choke
 - CCS (with μ -output)
 - Transformer

Filament Starvation

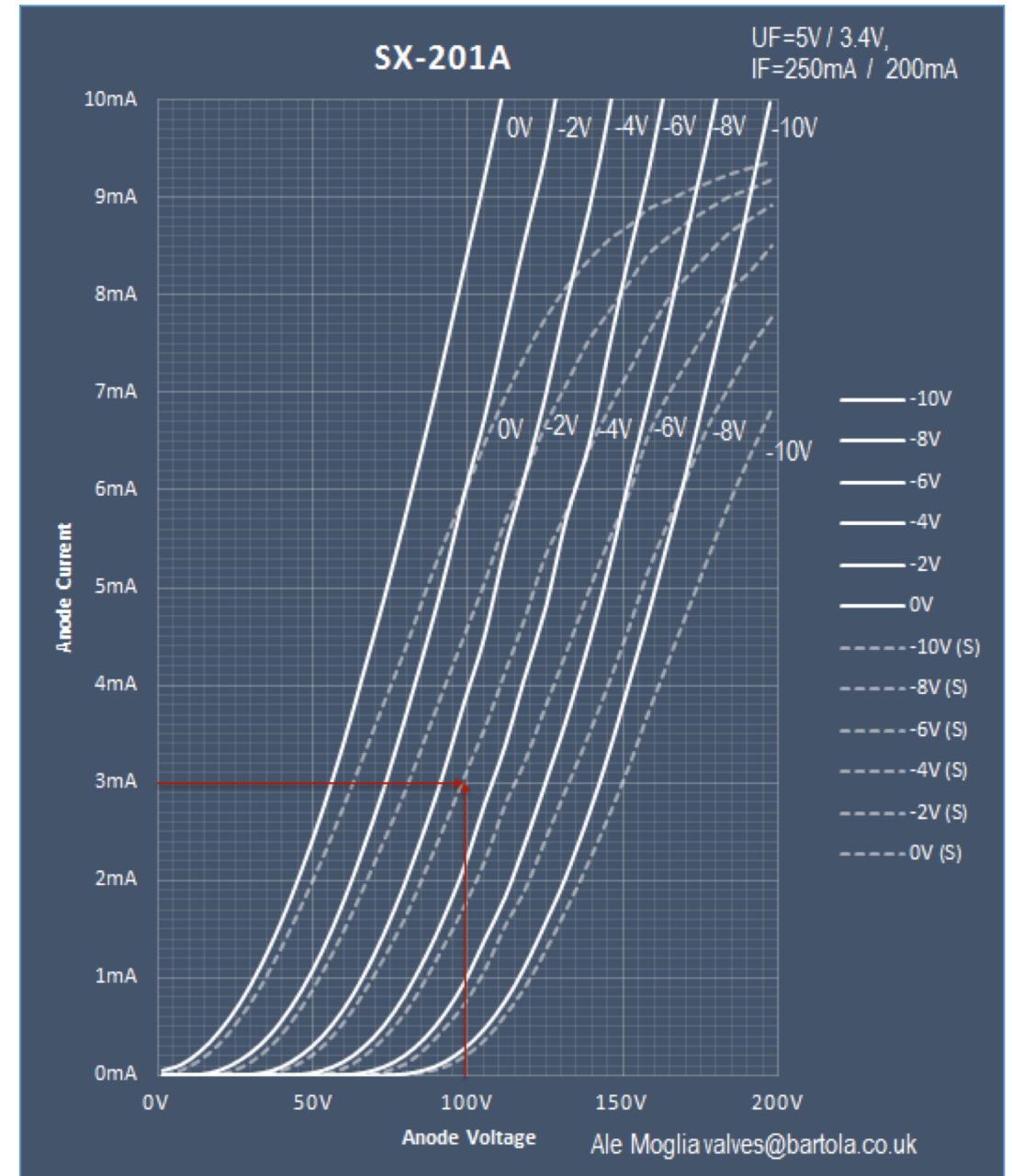
- Reduced microphonic noise
- Reduced emission
- Increased r_a , reduced g_m and (nearly) constant μ
- Reduced distortion
 - Increased region where g_m , r_a and μ are constant [5]
- Reduced valve life
 - Surface-level barium depletion (Oxide Fil)
 - “Cathode stripping” (TT filaments)



Bias Using SiC Diodes

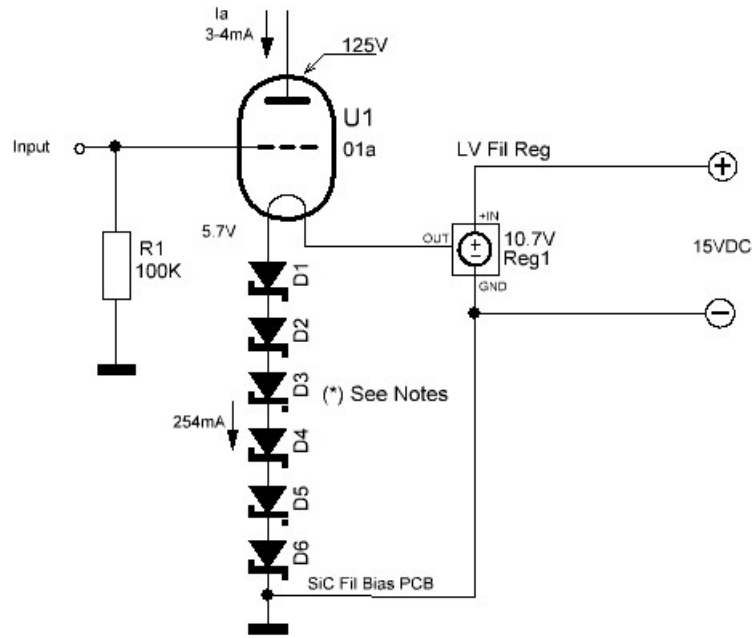


Filament SiC Bias

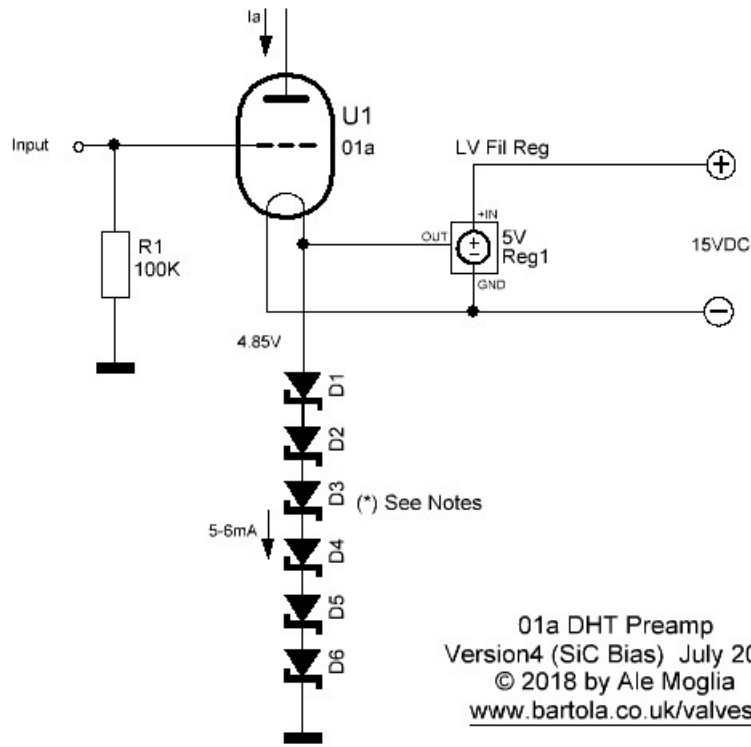


Cathode SiC Bias

01a DHT Preamp
Version4 (SiC Bias) July 2018
© 2018 by Ale Moglia
www.bartola.co.uk/valves


C3D02060F Example

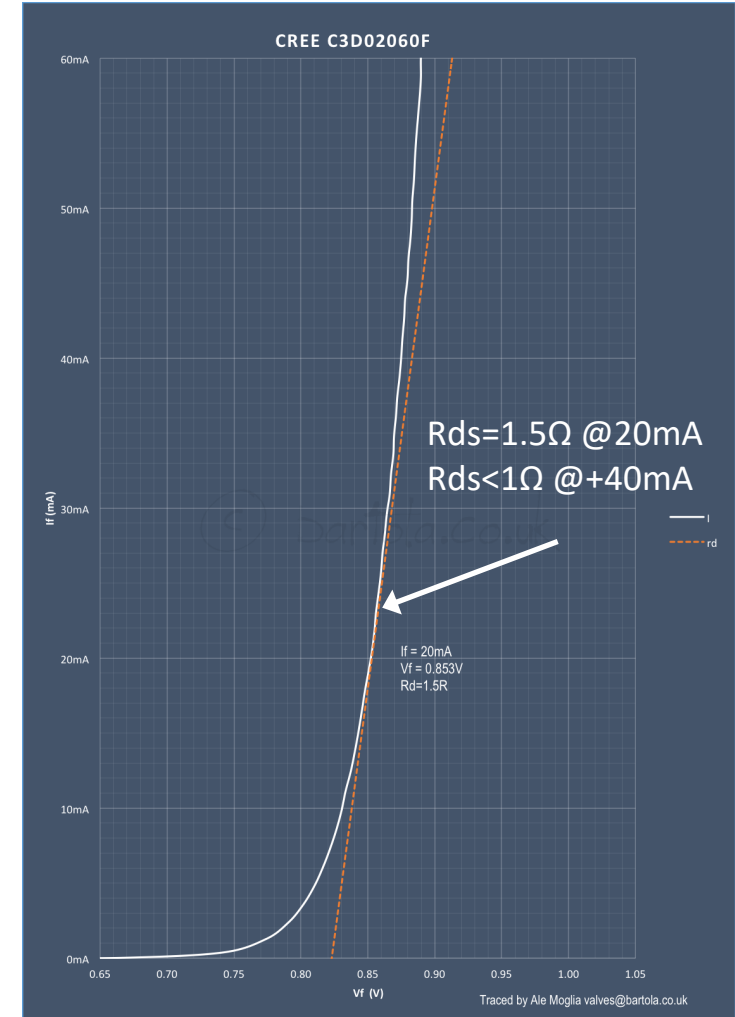


DHT Pre-amp Evolution

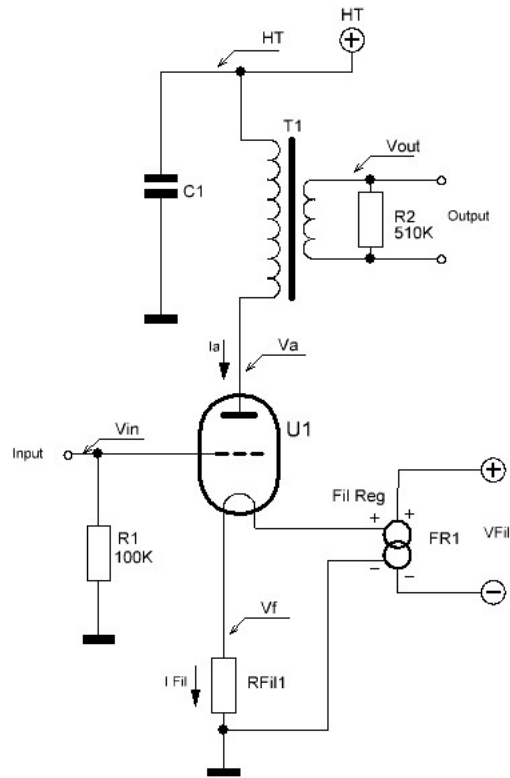

Transformer Loaded

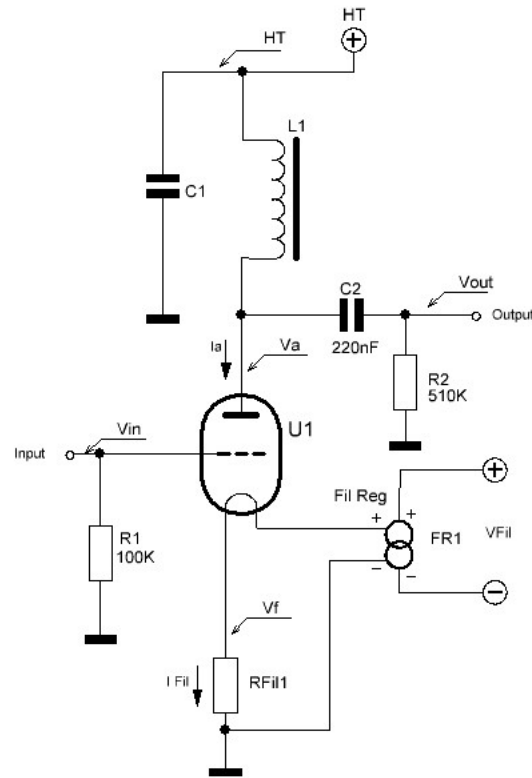


Choke Loaded

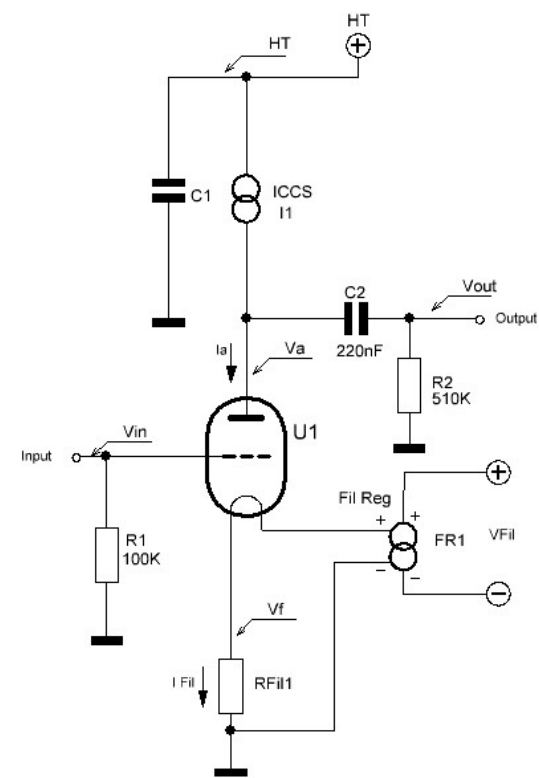

CCS Loaded

The μ -follower

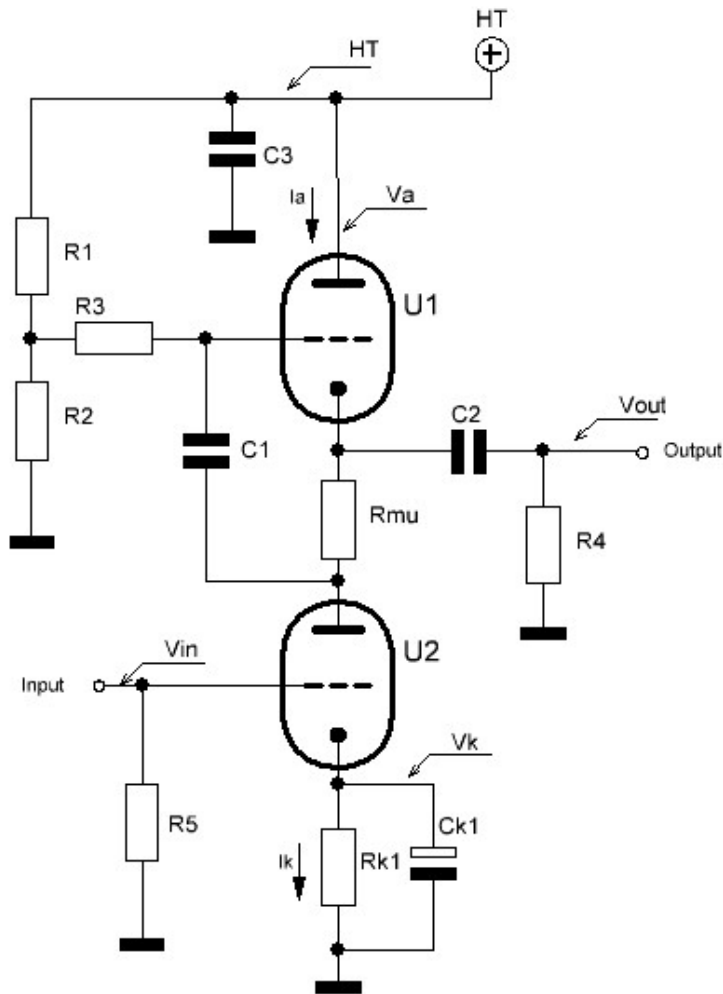


Advantages

- Push-pull
- Low output impedance
- Lowest distortion when optimized for specific load
- Higher bandwidth
- U1 Pentode: constant gm, lower distortion and better PSR

Disadvantages

- HT to accommodate full output swing
- Optimisation only for a specific load
- Heater supply (and elevation)
- The higher R_{μ} , the lower the current drive

The Hybrid μ -follower

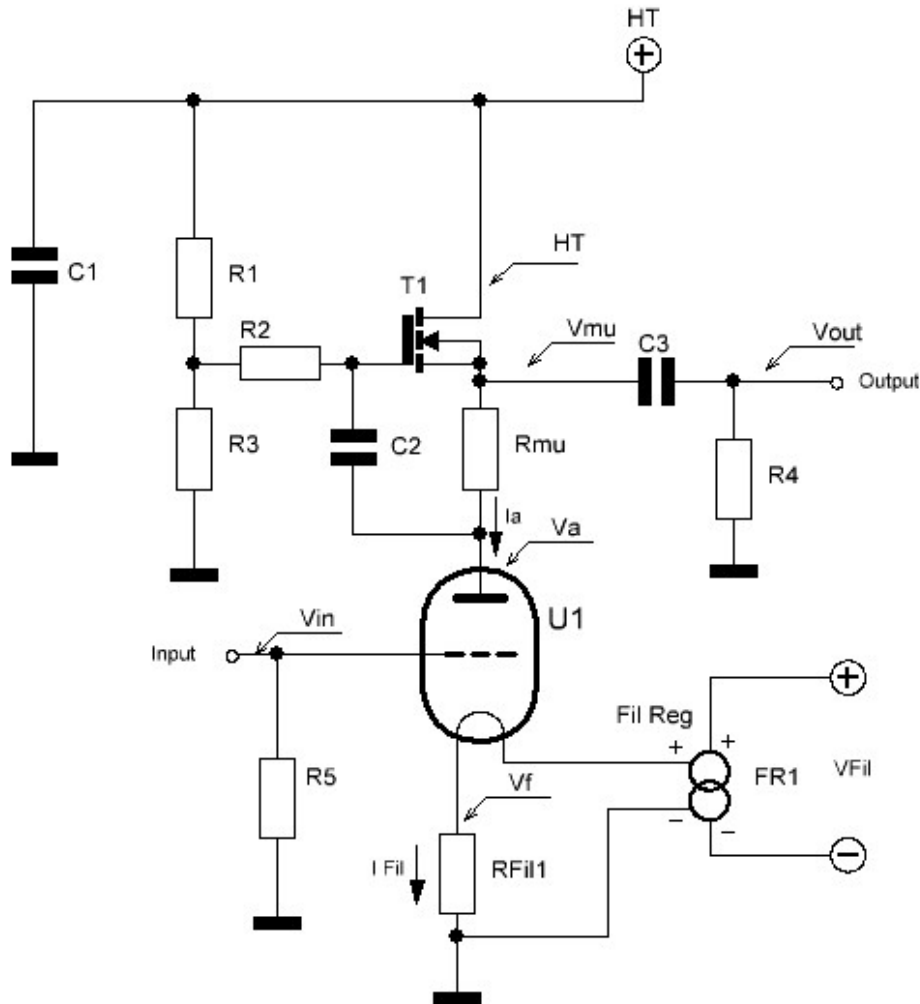


Advantages

- Use of higher gm part:
 - Lower output impedance
 - Lower distortion (R_{μ} bootstrapping)
- Simplified heater supply

Disadvantages


- MOSFETs protection
- Device Unbalance

The Hybrid μ -follower Evolution

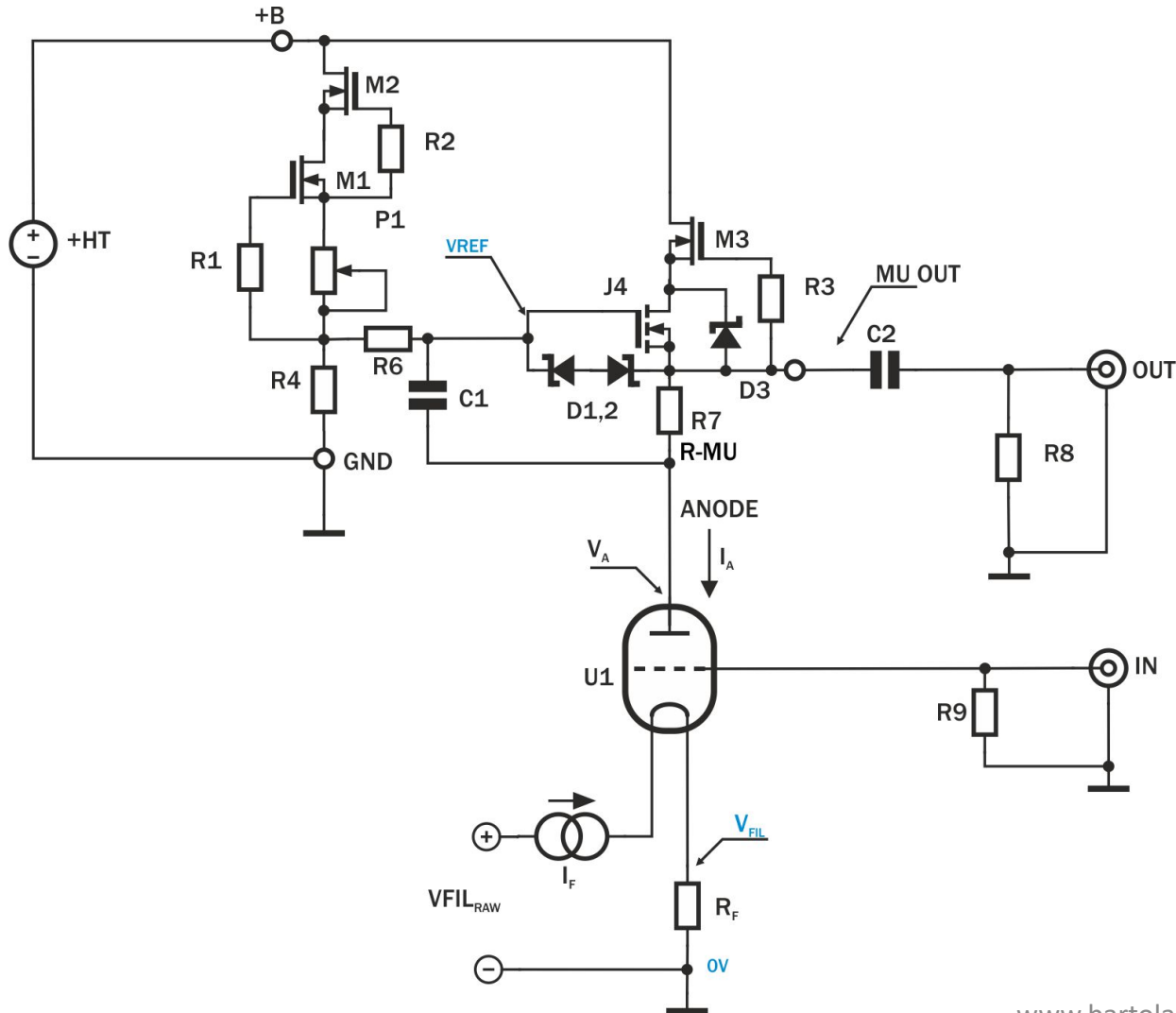


- CCS Voltage reference
 - Power supply isolation
 - Voltage stability
- Cascoded FET pair
- Improved HF response and lower output impedance:
 - J4: high G_f s and low C_{rss}
 - M3: High $V_{GS}(\text{off})$ -> reduce J4 C_{rss} and C_{oss}
- Keeping C1 value low


CCS vs Hybrid μ -follower

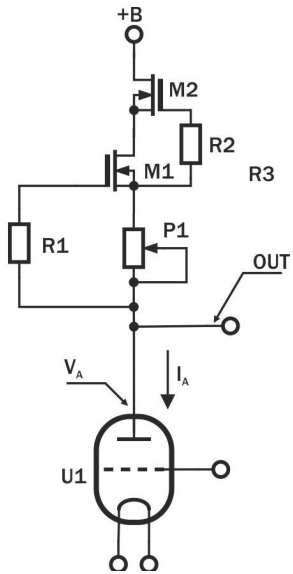

	CCS	Hybrid μ -Follower
Valve parameter fixed	Anode current	Anode Voltage
Output impedance	Mid-High (anode resistance)	Very Low ($1/gfs$)
Mode	Single-ended	Push-Pull
Complexity	Low	High
Low impedance loads	No	Yes


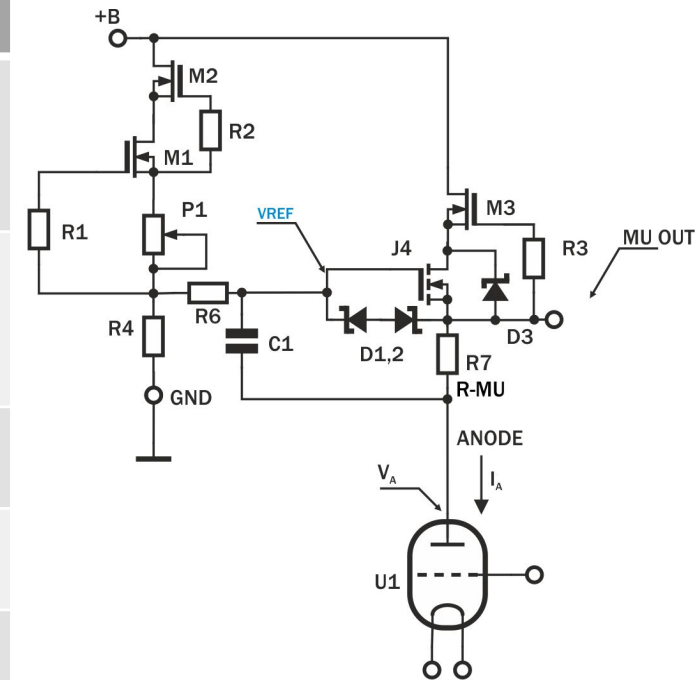


The CCS Reference Voltage

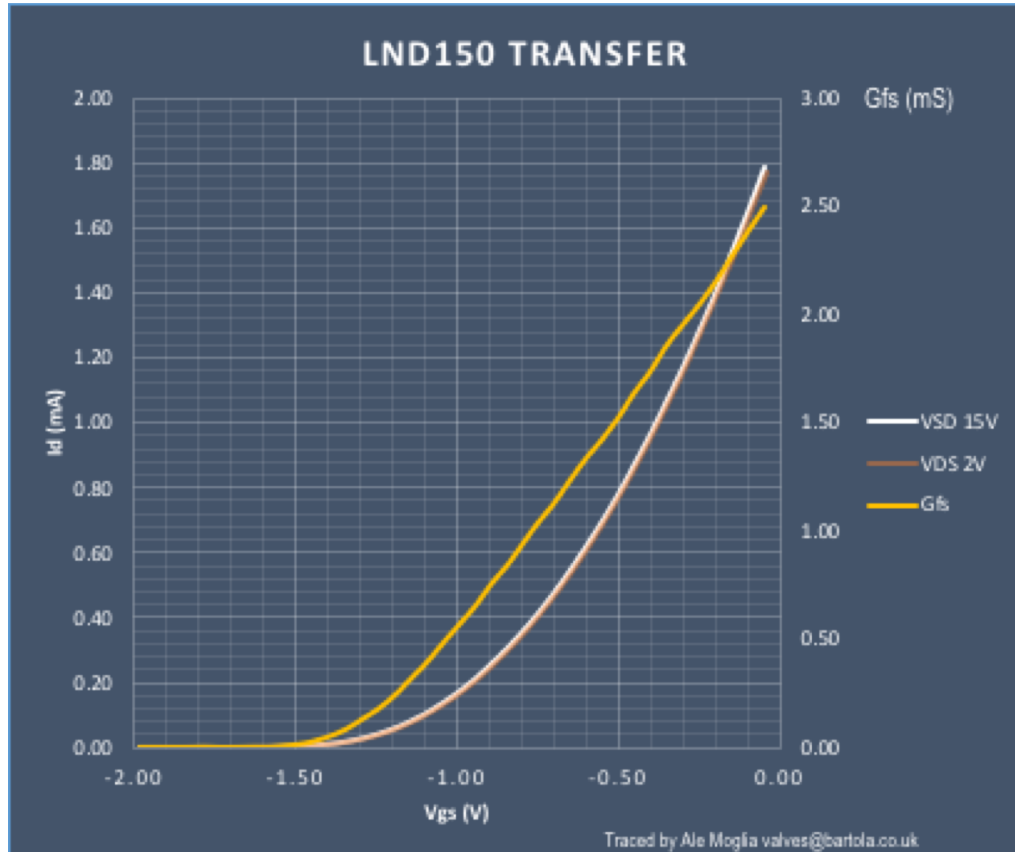


- Lowest TEMPCO [4] for LND150 measured:

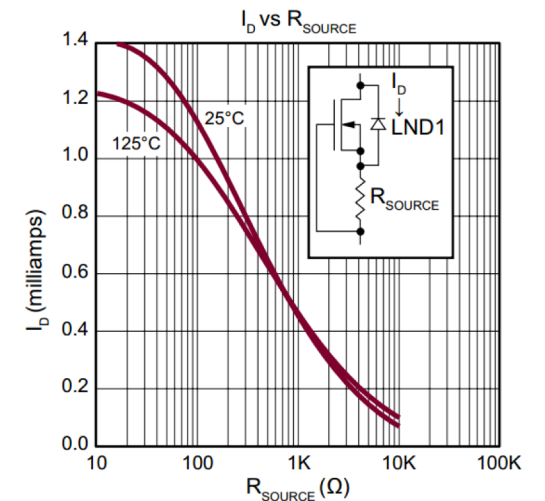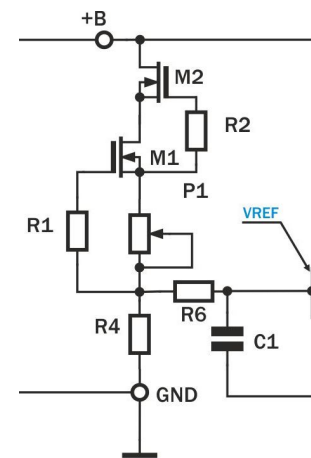- $V_{gs_{off}} = -1.6V$
- $I_{DSS} = 1.8mA$
- $V_{gs(0TC)} = V_{gs_{off}} - 0.63V = 0.97V$
- $I_{DZ} = I_{DSS} \cdot \left(\frac{0.63V}{V_{gs_{off}}}\right)^2 = 0.28mA \rightarrow$
- $R_S = \frac{V_{gs(0TC)}}{I_{DZ}} = 3.47K\Omega$



Some Math...

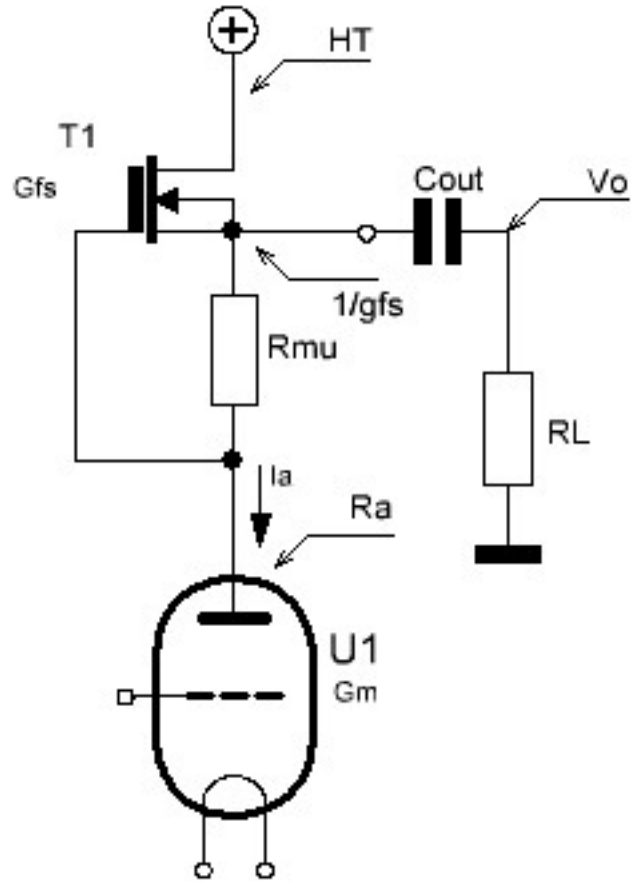

- For totem-pole current balance

$$g_{fs} = g_m \text{ so } R_\mu \cong \frac{1}{g_m}$$
 for current balance in the load


- Output impedance: $Z_O = \frac{R_a + R_\mu}{1 + R_\mu \cdot g_{fs}}$

- For a low R_a then $Z_O \cong \frac{1}{g_{fs}}$

FETs and MOSFETs: an Endless Tale


	LSK170	BF862 (*)	B5H111BK	DN2540	BSN20BK	BSP149	RU1C001UN
Ptot (W)	0.4	0.3	0.3	1	0.31	1.8	0.15
VDS	40	20	55	400	60	200	20
VGS off	2	-1.2		-1.5	1	-1.4	
IDSS (mA)	12	25	210	120	265	660	
Gfs (mS) (*)	22	45	640	300	710	800	180
Id Gfs (mA)	18	18	200	125	200	480	100
Id (mA)	10	10	10	10	10	10	10
Gfs @ Id (ms)	16	34	143	85	159	115	57
Ciss (pF)	20	10	19.1	200	20.2	326	7.1
Crss (pF)	5	1.9	1.5	1	2	17	1.7
Coss (pF)			2.7	12	3.1	41	3.3
1/gfs (ohms)	61	30	7	12	6	9	18

HV Depletion MOSFETs (Id vs Vgs)

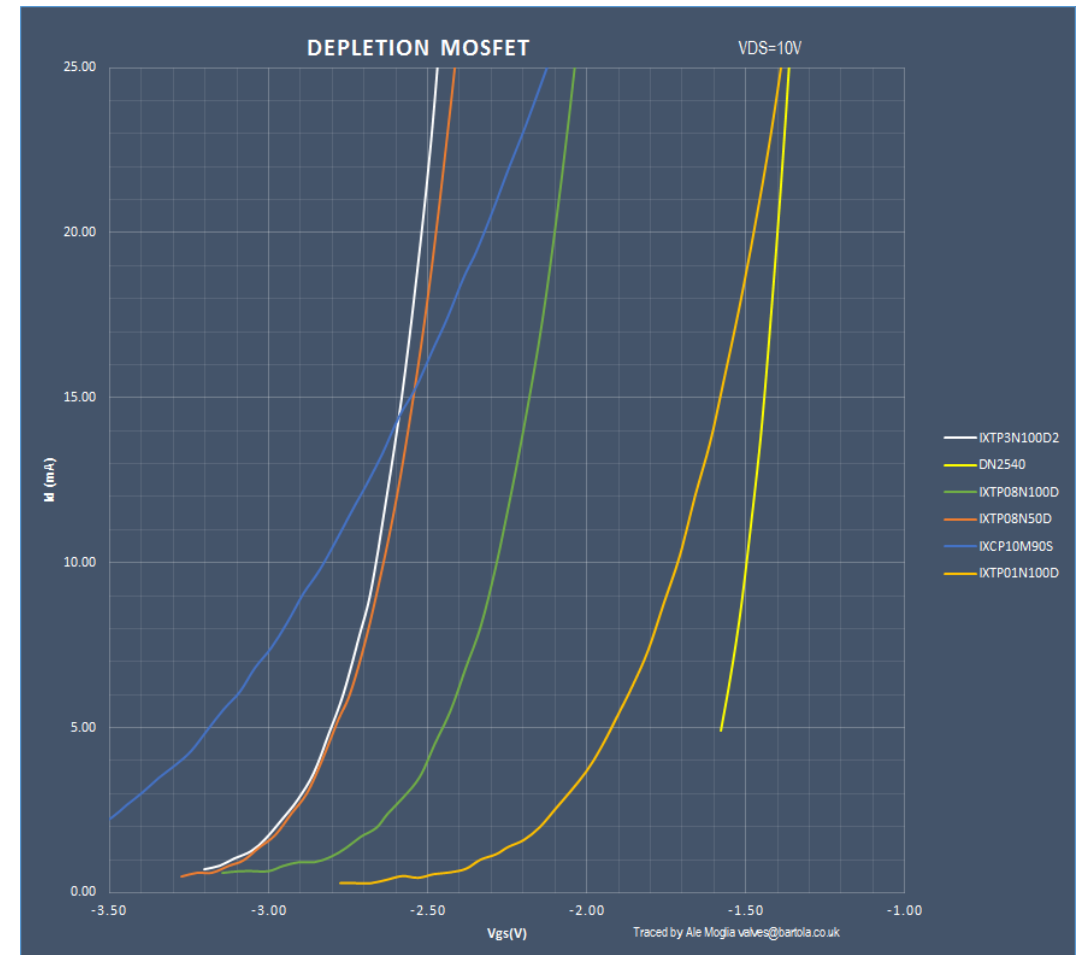

(*) EOL now, 2SK3557 and CPH3910 instead

Where To Place The Volume Control?

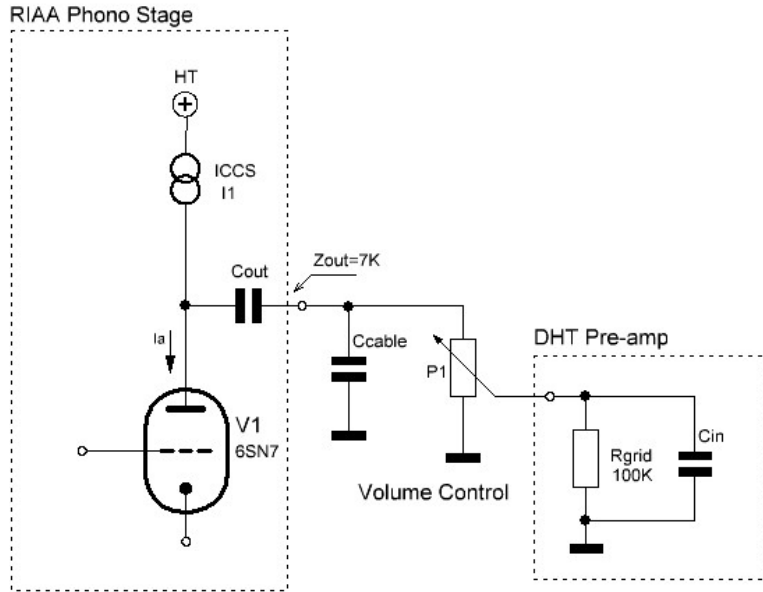


Can we use a 20K vol. control at the input of the DHT pre-amp?

Example 1

- Short interconnect cable ($C_{cable} \approx 200pF$)
- DHT preamp valve is 10/VT-25:
 - $C_{in} = C_{gk} + (\mu + 1) \cdot C_{ag} \approx 70pF$
- If volume control is 20K Ω (90% position):
 - $f_{-3dB} = 123kHz$
- If volume control is 100K Ω (90% position):
 - $f_{-3dB} = 98kHz$


Can You Drive Me?

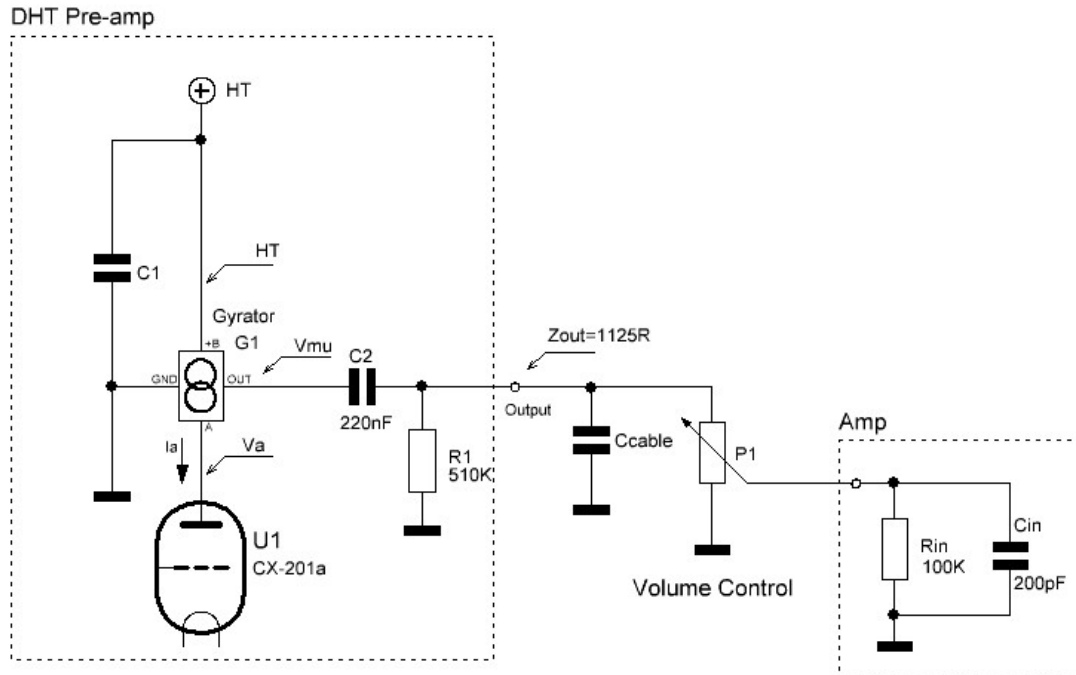

Can the DHT Pre-amp drive 5m cable?




- 5m interconnect: ($C_{cable} \approx 1.1nF$)
- CX-201a follower $R_{OUT} \cong 1125\Omega$ for $R_{\mu} = 470\Omega$ and $G_{fs} \cong 20mS$ @ $I_a = 3mA$
- If volume control is $20K\Omega$ (90% position):
 - $f_{-3dB} = 118kHz$
 - However, $C_2 \geq 1\mu F$ for $f_{-3dB} = 9Hz$
- Slew rate limitation:
 - $I_C = C \cdot 2\pi \cdot f \cdot V_{peak}$
 - If $I_A = 3mA$ and $V_{peak} = 10V$ then $f_{max} = \frac{I_A}{C \cdot 2\pi \cdot V_{peak}} = 36kHz$
 - For $f_{max} = 100kHz$ then $I_A = 8mA$.
 - Source or cathode follower solution

A Practical Example: 2P29L

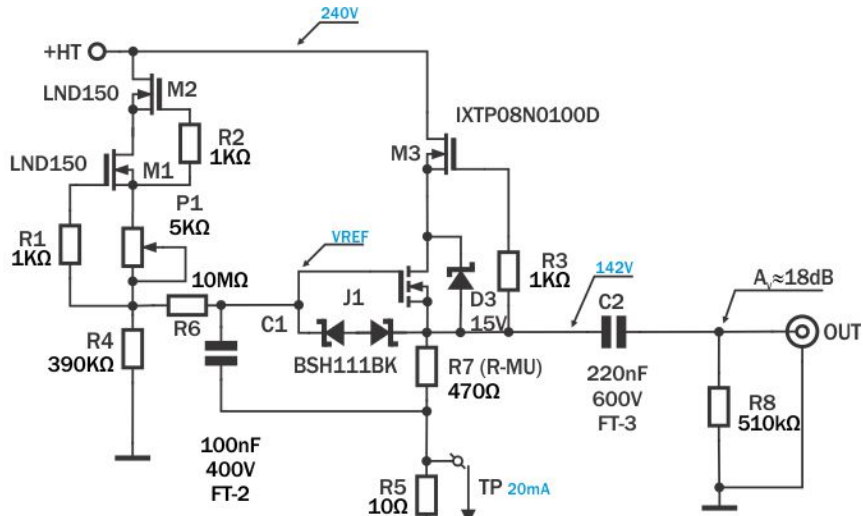

2P29L DHT Preamp

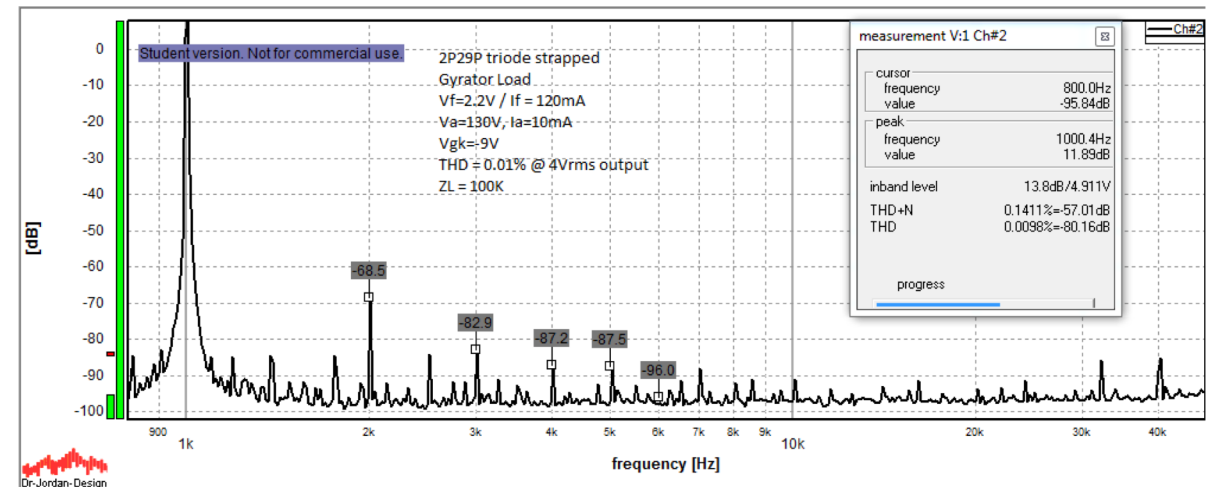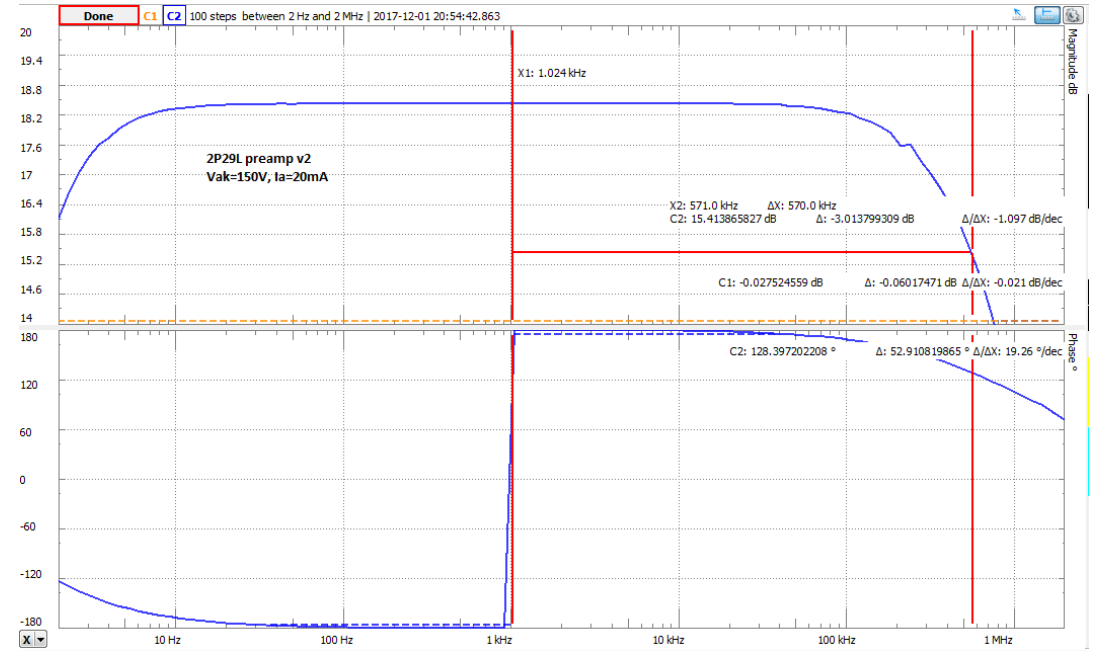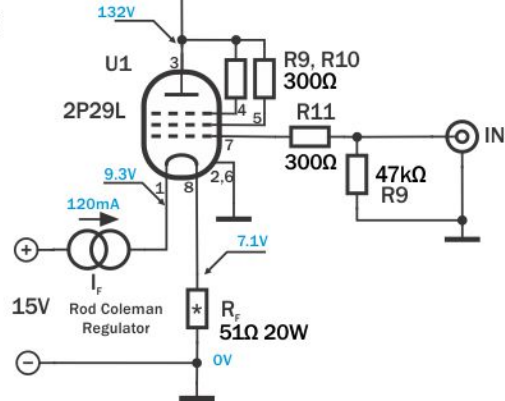Version 1 (20/05/17)
 © 2016-2017 Alejandro Moglia
 (for personal use only)
 valves@bartola.co.uk



Valve	Timbre & Detail	Microphony	Current Drive	Gain	Notes
801a 10-Y VT-25	● ● ●	●	●	M	<ul style="list-style-type: none"> Challenging for filament bias (heat) but doable Thoriated-tungsten filaments ER801a a great option!
01a	● ● ●	●	●	M	<ul style="list-style-type: none"> Be careful with old valves and microphonic devices Great for filament bias Thoriated-tungsten filaments
2P29L	● ●	●	●	M	<ul style="list-style-type: none"> Still cheap and plentiful Remove the aluminum can and use it naked! Great for filament bias
Aa / Ba	● ● ●	●	●	H	<ul style="list-style-type: none"> Rare and expensive Ba picks too much hum – needs shielding Good for gain but needs SF/CF stage
4P1L	● ●	●	●	M	<ul style="list-style-type: none"> Still available Easy to match pairs Can be very microphonic
26	● ●	●	●	M	<ul style="list-style-type: none"> Be careful with old valves and microphonic valves
199	● ● ●	●	●	M	<ul style="list-style-type: none"> Very microphonic Old and scarce, Variance between samples Short pin UV99/199
45 / 46	● ●	●	●	L	<ul style="list-style-type: none"> Bias levels prevents filament bias use Low gain
112a	●	●	●	M	<ul style="list-style-type: none"> Better current drive than 01a, but lack of thoriated tungsten filaments
RE-804	● ●	●	●	H	<ul style="list-style-type: none"> Hard to find in NOS. Valvo brand is best.
71a	●	●	●	L	<ul style="list-style-type: none"> Low μ and anode resistance. Ideal for line stage when gain isn't needed


Closing Note

- DHTs sound is unique and worth the trouble
- Don't underestimate role of power supplies
- Right topology for your system
- Don't be afraid of sand 😊



Acknowledgements

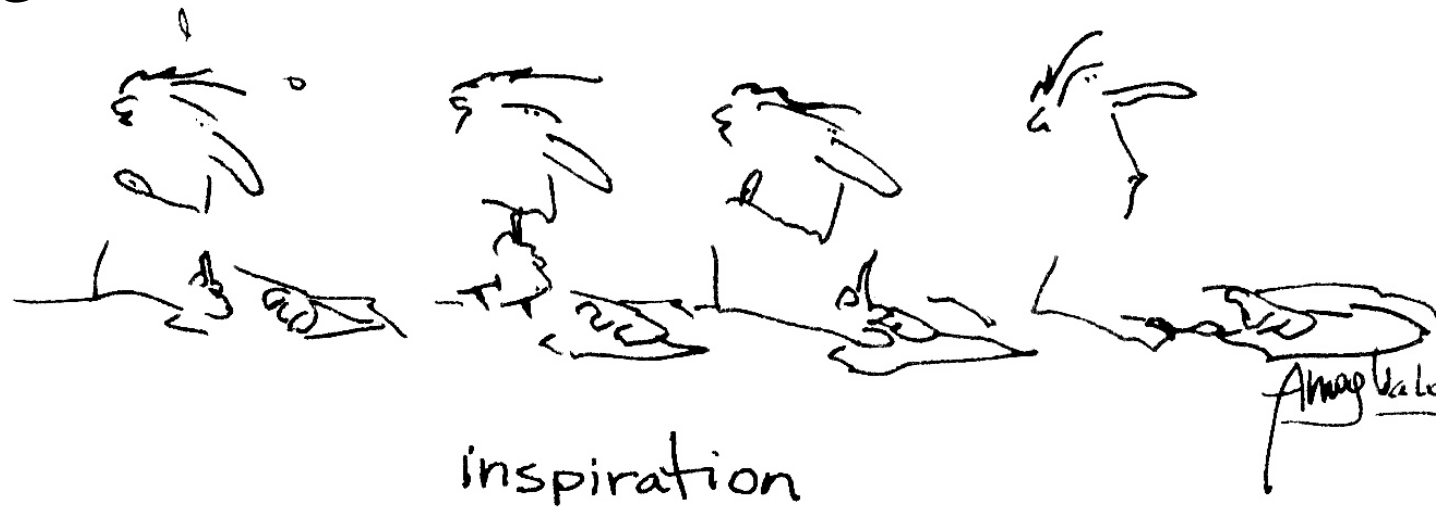- Morgan Jones
- Rod Coleman
- Andy Evans & Tony Rees
- Tom Browne



References

1. Alan Kimmel's "Mu Stage Philosophy" - <http://www.fetaudio.com/wp-content/uploads/2003/09/Mu-Stage.pdf>
2. Gary Pimm's website (archived)
3. Morgan Jones' "Building Valve Amplifiers"
4. Linden T. Harrison's "Current Sources & Voltage References"
5. Steve Bench's "Directly Heated Triodes operated with lower voltage on the filaments"
6. SRPP theory and evolution:
 1. John Broskie's "SRPP deconstructed", "SRPP+" - www.tubecad.com
 2. Merlin Blencowe's "The Optimised SRPP Amp" - http://www.valvewizard.co.uk/SRPP_Blencowe.pdf

Thank You!



Alejandro Moglia

www.bartola.co.uk/valves

valves@bartola.co.uk